



ÇANKAYA UNIVERSITY

Department of Mathematics and Computer Science

**PHYS 122 - General Physics II**

**FINAL EXAMINATION**

08.06.2010

**STUDENT NUMBER:**

**NAME-SURNAME:**

**SIGNATURE:**

**INSTRUCTOR:** Emre Sermutlu

**DURATION:** 90 minutes

Question	Grade	Out of
1		20
2		20
3		20
4		20
5		20
Total		100

**IMPORTANT NOTES:**

- 1) Please make sure that you have written your student number and name above.
- 2) Check that the exam paper contains 5 problems.
- 3) Show all your work. No points will be given to correct answers without reasonable work.

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N.m}^2, \quad \frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ N.m}^2/\text{C}^2$$

$$\text{Capacitor: } q = CV, \quad \text{Parallel Plate Capacitor: } C = \frac{\epsilon_0 A}{d}$$

$$\text{Energy Stored in a Capacitor: } U = \frac{1}{2}CV^2 = \frac{Q^2}{2C}$$

$$\text{Effect of Dielectric : } C = \kappa C_{air}$$

$$\text{Power in Electrical Device: } P = iV$$

$$\text{Charging a Capacitor: } q = C\mathcal{E}(1 - e^{-t/RC})$$

$$\text{Discharging a Capacitor: } q = q_0 e^{-t/RC}$$

$$\text{Magnetic Force on a Moving Particle: } \vec{F}_B = q\vec{v} \times \vec{B}$$

$$\text{Charged Particle Circulating in a Magnetic Field: } r = \frac{mv}{|q|B}$$

$$\text{Permeability Constant: } \mu_0 = 4\pi \times 10^{-7} \text{ Tm/A}$$

$$\text{Magnetic Field of a Long Straight Wire: } B = \frac{\mu_0 i}{2\pi R}$$

$$\text{Magnetic Field of a Circular Arc (at center): } B = \frac{\mu_0 i \phi}{4\pi R}$$

$$\text{Force Between Parallel Currents: } F_{ba} = \frac{\mu_0 I_a I_b}{2\pi d}$$

$$\text{Ampere's Law: } \oint \vec{B} \cdot d\vec{s} = \mu_0 I_{enc}$$

$$\text{Faraday's Law: } \mathcal{E} = -N \frac{d\Phi_B}{dt}$$

$$\text{Magnetic Energy of Inductor: } U = -\frac{1}{2}Li^2$$

$$\text{Impedance: } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{Phase constant: } \tan \phi = \frac{X_L - X_C}{R}$$

$$\text{Power in RLC circuit: } P_{avg} = \mathcal{E}_{rms} I_{rms} \cos \phi$$

$$\text{Capacitive Reactance: } \frac{1}{\omega C}, \quad \text{Inductive Reactance: } \omega L$$

$$\text{Ampere - Maxwell Law: } \oint \vec{B} \cdot d\vec{s} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt} + \mu_0 I_{enc}$$


$$\text{Displacement Current: } i_d = \epsilon_0 \frac{d\Phi_E}{dt}$$

$$\text{Plane Electromagnetic Wave: } \frac{E}{B} = c = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$$


$$\text{Poynting Vector: } \vec{S} = \frac{1}{\mu_0} \vec{E} \times \vec{B}$$

$$\text{Intensity: } I = \frac{1}{c\mu_0} E_{rms}^2$$

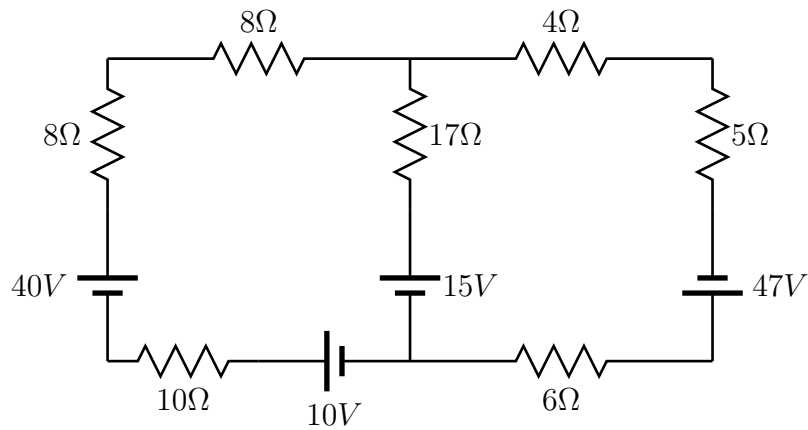1) Find all currents in the following circuit:



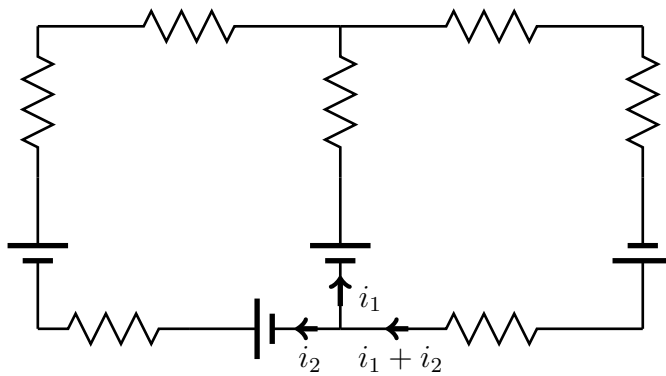**Answer:** Let's choose the currents as follows:



Now, using Kirchoff's loop rule, we obtain:

$$+10 - 10i_2 + 40 - 8i_2 - 8i_2 + 17i_1 - 15 = 0$$

$$+15 - 17i_1 - 4(i_1 + i_2) - 5(i_1 + i_2) + 47 - 6(i_1 + i_2) = 0$$

$$-17i_1 + 26i_2 = 35$$

$$32i_1 + 15i_2 = 62$$

The solution of this system of equations give:

$$i_1 = 1A, \quad i_2 = 2A, \quad i_1 + i_2 = 3A$$

2) a) The time constant of an  $RC$  circuit is  $\tau = RC = 0.05 \text{ s}$ . Find the time necessary for initially uncharged capacitor to be charged to 99% of its final charge.

**Answer:**

$$q = C\mathcal{E}(1 - e^{-t/RC})$$

Final charge is  $C\mathcal{E}$  therefore  $q = 0.99 C\mathcal{E}$ .

$$0.99 = 1 - e^{-t/\tau}$$

$$e^{-t/\tau} = 0.01$$

$$-t/\tau = \ln 0.01$$

$$t = 0.05\text{s} \times 4.6 = 0.23\text{s}.$$

b) A particle of mass  $m$ , charge  $q$  travels in a circular path of radius  $R$  in a uniform magnetic field  $B$ . Find its period of revolution.


**Answer:**

$$r = \frac{mv}{qB}$$

$$T = \frac{2\pi r}{v}$$

$$T = \frac{2\pi m}{qB}$$

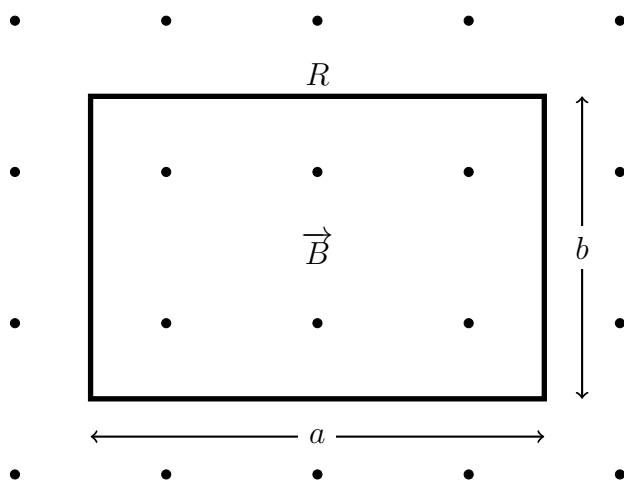- 3) A variable magnetic field of magnitude  $B = B_0(1 + t^3)$  is perpendicular to a rectangular loop. The loop has dimensions  $a \times b$  and resistance  $R$ . Find the magnitude and direction of the induced current.



**Answer:**

$$\Phi_B = BA = Bab = B_0(1 + t^3)ab$$

$$\mathcal{E} = -\frac{d\Phi_B}{dt} = -B_0 3t^2 ab$$

$$I = \frac{\mathcal{E}}{R} = -\frac{3B_0 t^2 ab}{R}$$

Positive direction is counter-clockwise.  
Therefore  $I$  is in clockwise direction.

- 4) a) In a series RLC circuit,  $L = 90\text{ mH}$ ,  $C = 1.5\text{ }\mu\text{F}$  and  $f = 0.8\text{ kHz}$ . If the phase constant is  $55^\circ$ , what is the resistance of the coil?

**Answer:**

$$\omega = 2\pi f = 5027\text{ s}^{-1}$$

$$X_L = \omega L = 452\text{ }\Omega$$

$$X_C = \frac{1}{\omega C} = 132\text{ }\Omega$$

$$\frac{X_L - X_C}{R} = \tan 55 = 1.428$$

$$R = \frac{X_L - X_C}{\tan \phi} = 224\text{ }\Omega$$

- b) An oscillating LC circuit is made of a  $4\text{ nF}$  capacitor and a  $9\text{ mH}$  inductor. The maximum current is  $3\text{ A}$ . What is the maximum charge on the capacitor?

$$\frac{1}{2}LI_{max}^2 = \frac{1}{2}\frac{q_{max}^2}{C}$$

$$q_{max} = \sqrt{LC} I$$

$$q_{max} = \sqrt{9 \cdot 10^{-3} \cdot 4 \cdot 10^{-9}} 3$$

$$q_{max} = 18\text{ }\mu\text{C}$$

- 5) a) The displacement current through a rectangular loop of area  $3.5 \text{ m}^2$  is  $8 \text{ A}$ . At what rate is the electric field through the loop changing?

$$i_d = \varepsilon_0 \frac{d\Phi_E}{dt} = \varepsilon_0 \frac{d(EA)}{dt} = \varepsilon_0 A \frac{dE}{dt}$$

$$\frac{dE}{dt} = \frac{i_d}{\varepsilon_0 A} = \frac{8}{8.85 \cdot 10^{-12} \cdot 3.5}$$

$$\frac{dE}{dt} = 2.58 \times 10^{11} \text{ V/m.s}$$

- b) The maximum electric field of an electromagnetic wave is  $5 \text{ V/m}$ . What is the intensity?

$$I = \frac{E_{rms}^2}{c\mu_0} = \frac{E_m^2}{2c\mu_0}$$

$$I = \frac{5^2}{2 \cdot 3 \cdot 10^8 \cdot 4\pi \cdot 10^{-7}}$$

$$I = 0.033 \text{ W/m}^2$$